
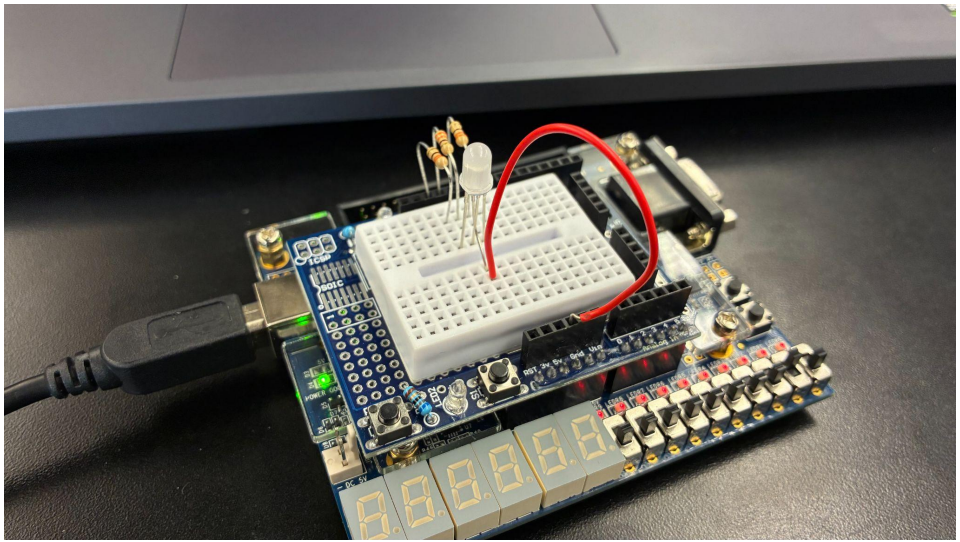
# Lab 8


Chelsea Sisneros

This is the RGB light connected. The red wire is connected to ground, the resistors are connected to pins 11-13.



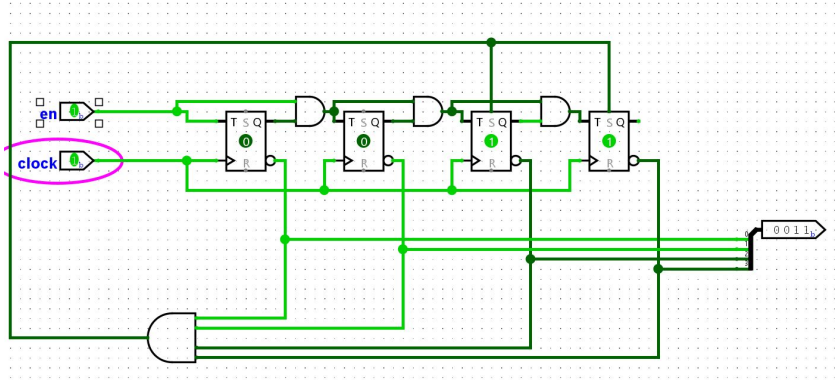
Started with a t-flip-flop counter. This one counts for 3 seconds, but it needs to count just 1 second.



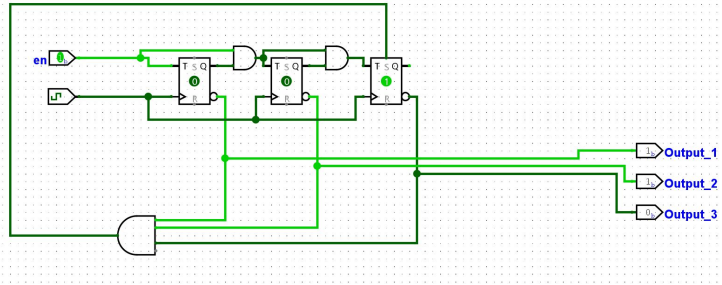


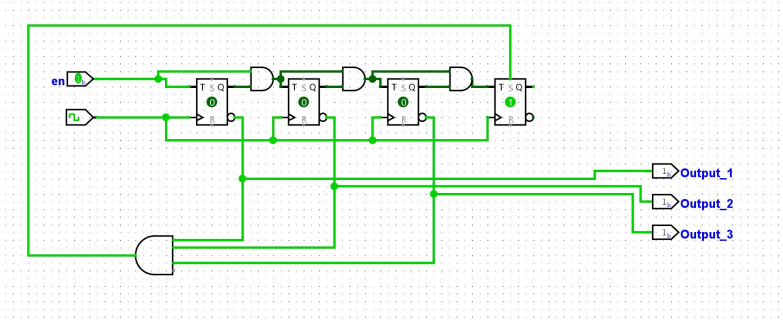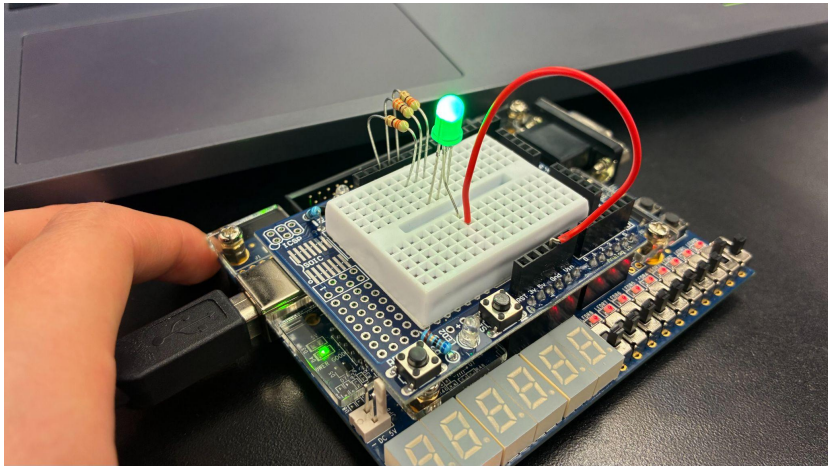
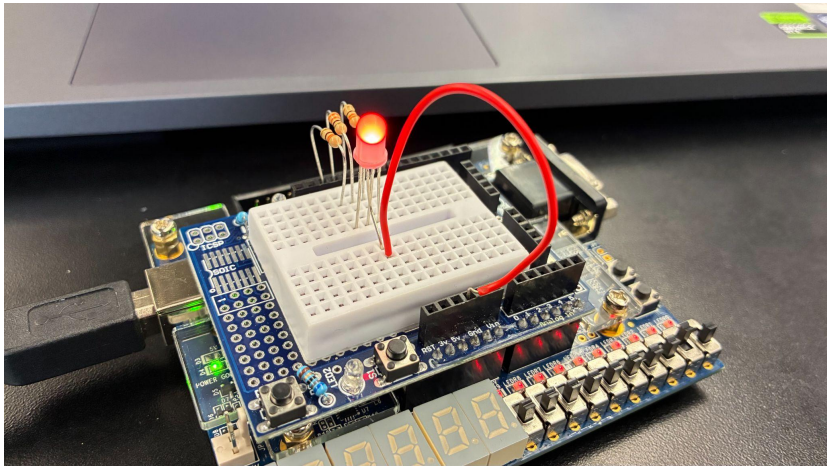

This has a clock, but it only cycles through 3 colors. Red, yellow, and green. This is because output 2 is not connected properly.

Cycling 8 patterns at 1 second.





I ended up needing the fourth t-flip-flop. This allowed 8 of the colors on the LED cycle!





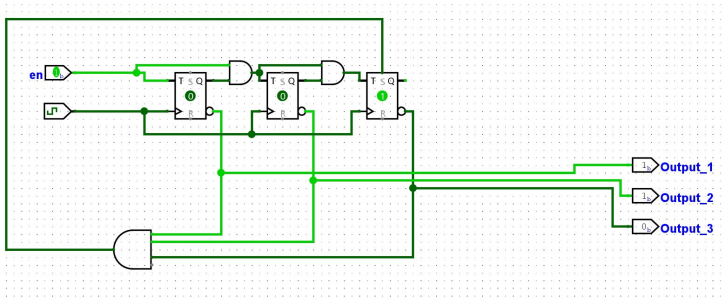To do the second project, I found that if Output_2 =  0 and Output_1 = 1, the LED cycles red. The clock allows the red LED to turn on and off for about a second.




To do the second project, I found that if Output_2 =  1 and Output_1 = 1, the LED cycles green. The clock allows the green LED to turn on and off for about a second. I just haven't figured out how to only get these to cycle on two different outputs.

I am a little confused on the multiplexers still. The solution shown on the board makes sense because the splitters cut off for each number, and using the input allows you to add as many inputs as possible.